

TRAFFIC LIGHT CONTROLLER USING FINITE STATE MACHINE

EECT / CE 6325 – VLSI DESIGN

Instructor

Prof. Carl Sechen

Submitted by

Ganesh Manjunath

Net ID: dal542146

&

Aryan Verma

Net ID: dal820508

Date: 09/24/2025

INTRODUCTION

Traffic management is a crucial aspect of modern day infrastructure, ensuring the safe and efficient movement of vehicles and pedestrians. Old traffic light systems rely on fixed timers, which often fail to adapt to complex traffic conditions. With the growth of smart cities, there is a strong need for intelligent traffic control mechanisms that are reliable, scalable, and hardware efficient.

Finite State Machines (FSMs) provide an effective way to model sequential behavior in digital systems, making them well-suited for traffic signal controllers. By defining distinct states—such as green, yellow, and red phases for both North-South (NS) and East-West (EW) directions—an FSM can accurately represent real-world traffic flow transitions. Implementing such a design in Verilog allows for simulation, verification, and eventual hardware realization using FPGA or ASIC technology.

This project discusses designing a traffic light controller using Verilog HDL, based on the Finite state machine approach. The design not only elaborates the systematic state transitions of a basic controller but also integrates features like parameterization, pulse-width modulation (PWM) for light intensity control, and scalability through different modules.. The work emphasizes hardware mapping & synthesizability, providing insight into practical VLSI design flow and digital system implementation.

Verilog Code

```
module traffic_light_controller #(
    parameter integer GREEN_TIME = 3000,
    parameter integer YELLOW_TIME = 500,
    parameter integer CWIDTH = 256,
    parameter integer UNIQUE_ID = 0
)(
    input wire clk,
    input wire rst,
    input wire sensor,
    output reg NS_Red,
    output reg NS_Yellow,
    output reg NS_Green,
    output reg EW_Red,
    output reg EW_Yellow,
    output reg EW_Green
);

localparam [3:0] S_NS_G = 4'b0001,
                S_NS_Y = 4'b0010,
                S_EW_G = 4'b0100,
                S_EW_Y = 4'b1000;

reg [3:0] state, next_state;
reg [CWIDTH-1:0] counter, next_counter;
reg [7:0] unique_reg;

always @(posedge clk) begin
    if (rst) unique_reg <= 8'b00000000;
    else unique_reg <= unique_reg + UNIQUE_ID;
```

```

end

always @(posedge clk) begin
    if (rst) begin
        state <= S_NS_G;
        counter <= {CWIDTH{1'b0}};
    end else begin
        state <= next_state;
        counter <= next_counter;
    end
end

always @* begin
    next_state = state;
    next_counter = counter + {{(CWIDTH-1){1'b0}},1'b1};
    case (state)
        S_NS_G: if (counter >= GREEN_TIME-1) begin next_state=S_NS_Y;
next_counter={CWIDTH{1'b0}}; end
        S_NS_Y: if (counter >= YELLOW_TIME-1) begin next_state=S_EW_G;
next_counter={CWIDTH{1'b0}}; end
        S_EW_G: if (counter >= GREEN_TIME-1) begin next_state=S_EW_Y;
next_counter={CWIDTH{1'b0}}; end
        S_EW_Y: if (counter >= YELLOW_TIME-1) begin next_state=S_NS_G;
next_counter={CWIDTH{1'b0}}; end
        default: begin next_state=S_NS_G; next_counter={CWIDTH{1'b0}}; end
    endcase
end

always @* begin
    NS_Red=0; NS_Yellow=0; NS_Green=0;
    EW_Red=0; EW_Yellow=0; EW_Green=0;

```

```

    case (state)
        S_NS_G: begin NS_Green=1; EW_Red=1; end
        S_NS_Y: begin NS_Yellow=1; EW_Red=1; end
        S_EW_G: begin EW_Green=1; NS_Red=1; end
        S_EW_Y: begin EW_Yellow=1; NS_Red=1; end
        default: begin NS_Green=1; EW_Red=1; end
    endcase
end

endmodule

module pwm #(
    parameter integer BITS = 256
)(
    input wire clk,
    input wire rst,
    input wire [BITS-1:0] duty,
    output reg y
);
    reg [BITS-1:0] cnt;
    always @(posedge clk) begin
        if (rst) cnt <= {BITS{1'b0}};
        else    cnt <= cnt + {{(BITS-1){1'b0}},1'b1};
    end
    always @* y = (cnt < duty);
endmodule

module ctl_with_pwm #(
    parameter integer GREEN_TIME = 3000,
    parameter integer YELLOW_TIME = 500,

```

```

parameter integer CWIDTH    = 256,
parameter integer PWM_BITS  = 256,
parameter integer UNIQUE_ID = 0
)(
    input wire clk,
    input wire rst,
    input wire sensor,
    output wire NS_Red, NS_Yellow, NS_Green,
    output wire EW_Red, EW_Yellow, EW_Green
);

wire nsr, nsy, nsy, ewr, ewy, ewg;

traffic_light_controller #(
    .GREEN_TIME(GREEN_TIME), .YELLOW_TIME(YELLOW_TIME),
    .CWIDTH(CWIDTH), .UNIQUE_ID(UNIQUE_ID)
) u_ctl (
    .clk(clk), .rst(rst), .sensor(sensor),
    .NS_Red(nsr), .NS_Yellow(nsy), .NS_Green(nsg),
    .EW_Red(ewr), .EW_Yellow(ewy), .EW_Green(ewg)
);

localparam [PWM_BITS-1:0] FULL = {PWM_BITS{1'b1}};

pwm #(.BITS(PWM_BITS)) p0(.clk(clk), .rst(rst), .duty(nsr ? FULL : {PWM_BITS{1'b0}}),
.y(NS_Red));

pwm #(.BITS(PWM_BITS)) p1(.clk(clk), .rst(rst), .duty(nsy ? FULL : {PWM_BITS{1'b0}}),
.y(NS_Yellow));

pwm #(.BITS(PWM_BITS)) p2(.clk(clk), .rst(rst), .duty(nsg ? FULL : {PWM_BITS{1'b0}}),
.y(NS_Green));

pwm #(.BITS(PWM_BITS)) p3(.clk(clk), .rst(rst), .duty(ewr ? FULL : {PWM_BITS{1'b0}}),
.y(EW_Red));

```

```
pwm #(.BITS(PWM_BITS)) p4(.clk(clk), .rst(rst), .duty(ewy ? FULL : {PWM_BITS{1'b0}}),  
.y(EW_Yellow));
```

```
pwm #(.BITS(PWM_BITS)) p5(.clk(clk), .rst(rst), .duty(ewg ? FULL : {PWM_BITS{1'b0}}),  
.y(EW_Green));
```

```
endmodule
```

```
module big_system #(  
    parameter integer N          = 200,  
    parameter integer GREEN_TIME = 3000,  
    parameter integer YELLOW_TIME = 500,  
    parameter integer CWIDTH     = 256,  
    parameter integer PWM_BITS   = 256  
)(  
    input wire          clk,  
    input wire          rst,  
    input wire [N-1:0]  sensor,  
    output wire [N-1:0] NS_Red, NS_Yellow, NS_Green,  
    output wire [N-1:0] EW_Red, EW_Yellow, EW_Green  
);  
  
genvar i;  
  
generate  
    for (i=0; i<N; i=i+1) begin : G  
        ctl_with_pwm #(  
            .GREEN_TIME(GREEN_TIME), .YELLOW_TIME(YELLOW_TIME),  
            .CWIDTH(CWIDTH), .PWM_BITS(PWM_BITS),  
            .UNIQUE_ID(i)  
        ) u (  
            .clk(clk), .rst(rst), .sensor(sensor[i]),  
            .NS_Red(NS_Red[i]), .NS_Yellow(NS_Yellow[i]), .NS_Green(NS_Green[i]),
```

```

        .EW_Red(EW_Red[i]), .EW_Yellow(EW_Yellow[i]), .EW_Green(EW_Green[i])
    );
end
endgenerate
endmodule

```

Testbench

```

`timescale 1ns/1ps

module traffic_light_controller_tb;

    // ---- Tunables ----

    localparam integer CLK_PER_NS = 10; // 100 MHz
    localparam integer RESET_CYCLES = 10; // hold reset this many cycles
    localparam integer RUN_CYCLES = 4000; // main stimulus length

    // ---- DUT I/O ----

    reg clk, rst, sensor;

    wire NS_Red, NS_Yellow, NS_Green;
    wire EW_Red, EW_Yellow, EW_Green;

    // Instantiate DUT (matches your gate netlist top)
    traffic_light_controller dut (
        .clk(clk), .rst(rst), .sensor(sensor),
        .NS_Red(NS_Red), .NS_Yellow(NS_Yellow), .NS_Green(NS_Green),
        .EW_Red(EW_Red), .EW_Yellow(EW_Yellow), .EW_Green(EW_Green)
    );

    // ---- Clock ----

    initial begin
        clk = 1'b0;

        forever #(CLK_PER_NS/2) clk = ~clk;
    end
end

```



```

// ---- Optional waveform dump (VCD for non-ModelSim tools) ----
`ifdef VCD
    initial begin
        $dumpfile("traffic_light_controller_tb.vcd");
        $dumpvars(0, traffic_light_controller_tb);
    end
`endif

// ---- Stimulus + heartbeat + basic checks ----
integer i;
initial begin
    $timeformat(-9,0," ns",10);
    $display("** TB start @ %0t **", $realtime);
    rst = 1'b1;
    sensor = 1'b0;

    // reset
    for (i = 0; i < RESET_CYCLES; i = i + 1) @(posedge clk);
    rst = 1'b0;

    // main run
    for (i = 0; i < RUN_CYCLES; i = i + 1) begin
        @(posedge clk);
        // deterministic activity on 'sensor' (avoids $random quirks)
        sensor <= sensor ^ NS_Green ^ EW_Green ^ NS_Yellow ^ EW_Yellow;


        // heartbeat every 500 cycles so you see progress in Transcript
        if ((i % 500) == 0)
            $display("%0t: heartbeat (i=%0d) NS[G,Y,R]=%0b%0b%0b EW[G,Y,R]=%0b%0b%0b",
                $realtime, i, NS_Green, NS_Yellow, NS_Red, EW_Green, EW_Yellow, EW_Red);

        // simple safety check: never both greens high in the same cycle
    end
end


```

```
if (!rst && (NS_Green & EW_Green)) begin
    $display("ERROR @ %0t: Both NS and EW GREEN!", $realtime);
    $stop;
end
end
$display("*** TB finish @ %0t ***", $realtime);
$finish;
end
endmodule
```

Waveform from the Behavioral code:

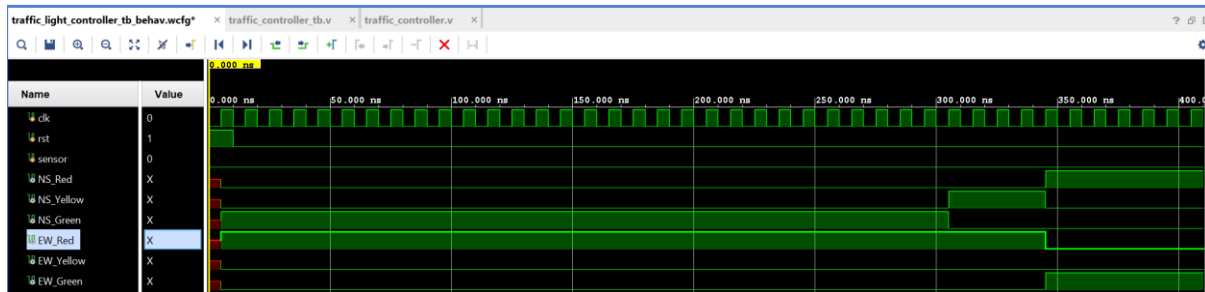

Waveform from the Mapped Code:

 

The Behavioral and mapped simulation waveforms of the traffic light controller match, confirming that the synthesized design preserves the intended functionality. The outputs transition correctly between North-South and East-West signals, validating both design and implementation.

Report from Design Vision

Report : cell

Design : traffic_light_controller

Version: O-2018.06-SP1

Date : Wed Sep 24 14:17:08 2025

Attributes:

b - black box (unknown)

h - hierarchical

n - noncombinational

r - removable

u - contains unmapped logic

Cell	Reference	Library	Area	Attributes

C283	nand2	library	1.000000	
C284	nand2	library	1.000000	
C288	nand2	library	1.000000	
C289	nand2	library	1.000000	
C293	nand2	library	1.000000	
C294	nand2	library	1.000000	
C298	nand2	library	1.000000	
C299	nand2	library	1.000000	
C1636	nand2	library	1.000000	
C1637	nand2	library	1.000000	

C1641	nand2	library	1.000000
C1642	nand2	library	1.000000
C1646	nand2	library	1.000000
C1647	nand2	library	1.000000
C1651	nand2	library	1.000000
C1652	nand2	library	1.000000
I_1	inv	library	1.000000
I_2	inv	library	1.000000
I_3	inv	library	1.000000
I_4	inv	library	1.000000
I_5	inv	library	1.000000
I_6	inv	library	1.000000
I_7	inv	library	1.000000
I_8	inv	library	1.000000
I_14	inv	library	1.000000
I_15	inv	library	1.000000
I_16	inv	library	1.000000
I_17	inv	library	1.000000
U268	oai12	library	2.000000
U269	inv	library	1.000000
U270	inv	library	1.000000
U271	inv	library	1.000000
U272	nand2	library	1.000000
U273	inv	library	1.000000
.			
.			
U1648	inv	library	1.000000

U1649	xor2	library	3.000000
U1650	xor2	library	3.000000
.			
U1903	xor2	library	3.000000
U1904	nand2	library	1.000000
.			
U1966	nand2	library	1.000000
U1967	inv	library	1.000000
.			
U2604	inv	library	1.000000
counter_reg[0]	dff	library	7.000000 n
.			
counter_reg[255]	dff	library	7.000000 n
r88/ULTI1	nand2	library	1.000000
r88/ULTI1_1	nand2	library	1.000000
.			
r89/ULTI2_254	nand2	library	1.000000
state_reg[0]	dff	library	7.000000 n
state_reg[1]	dff	library	7.000000 n
state_reg[2]	dff	library	7.000000 n
state_reg[3]	dff	library	7.000000 n

Total 3631 cells	5709.000000
------------------	-------------

Activities Design Vision - TopLevel.1 Sep 24 13:51

Design Vision - TopLevel.1 (traffic_light_controller)

File Edit View Select Highlight List Hierarchy Design Attributes Schematic Timing Test Power AnalyzeRTL Window Help

traffic_light_controller

Hier.1

Logical Hierarchy

Cells (Hierarchical)

Cell Name	Ref Name
-----------	----------

Report.7 - Cell

Report : cell
Design : traffic_light_controller
Version : 0-2018.06-SP1
Date : Wed Sep 24 13:47:36 2025

Attributes:

- b - black box (unknown)
- h - hierarchical
- n - noncombinational
- r - removable

Hier.1

Report.7

state_reg[1]	dff	library	7.000000	n
state_reg[2]	dff	library	7.000000	n
state_reg[3]	dff	library	7.000000	n

Total 3631 cells			5709.000000	
design_vision>				

Log History

design_vision>

Ready